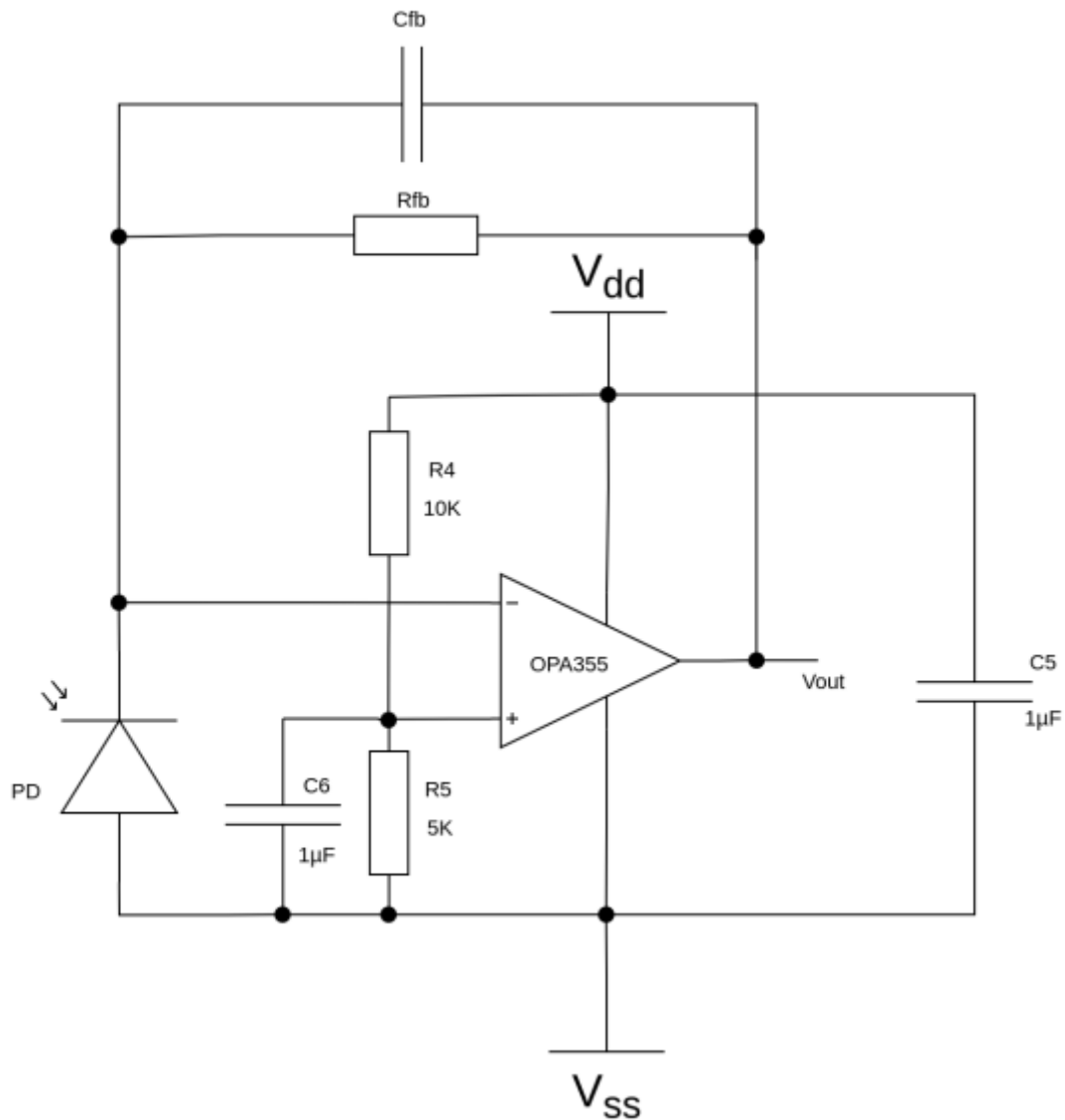


Task:

- Describe this transimpedance-amplifier circuit – how does it work? What is the task of every single component?
- Simulate the circuit with different (dynamically changing) input currents from the photodiode.



You can use:

V_{DD} = 3.3V

V_{SS} = Gnd (0V)

Rfb = 10 Mohm

Cfb = 0.2pF

Try to approximate the OPA355 behavior by using the datasheet of it.

The photodiode can be assumed as the OSRAM LW VH8G